

# AN1982

## Applying the oscillator of the SA602A in low-power mixer applications

Rev. 2 — 29 August 2014

Application note

### Document information

Info	Content
<b>Keywords</b>	Gilbert cell mixer, LC tank circuit, dual gate MOSFET, Colpitts oscillator.
<b>Abstract</b>	This application note discusses applying the oscillator of the SA602A in low power mixer applications. The SA602A consists of a Gilbert cell mixer, a buffered emitter follower oscillator, and RF current and voltage regulator. The simplicity of the oscillator affords many configurations which may be easily implemented to achieve good performance at frequencies to 500 MHz.



## Revision history

Rev	Date	Description
2	20140829	Application note; second release Modifications: <ul style="list-style-type: none"><li>• SA602 replaced with SA602A</li></ul>
1.0	19971023	Application note; initial release

## Contact information

For more information, please visit: <http://www.nxp.com>


For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

## 1. Introduction

For the designer of low power RF systems, the NXP Semiconductors SA602A mixer/oscillator provides mixer operation beyond 500 MHz, a versatile oscillator capable of operation to 200 MHz, and conversion gain, with only 2.5 mA total current consumption. With a proper understanding of the oscillator design considerations, the SA602A can be put to work quickly in many applications.

## 2. Description

[Figure 1](#) shows the equivalent circuit of the device. The chip is actually three subsystems: A Gilbert cell mixer (which provides differential input gain), a buffered emitter follower oscillator, and RF current and voltage regulation. Complete integration of the DC bias permits simple and compact application. The simplicity of the oscillator permits many configurations.

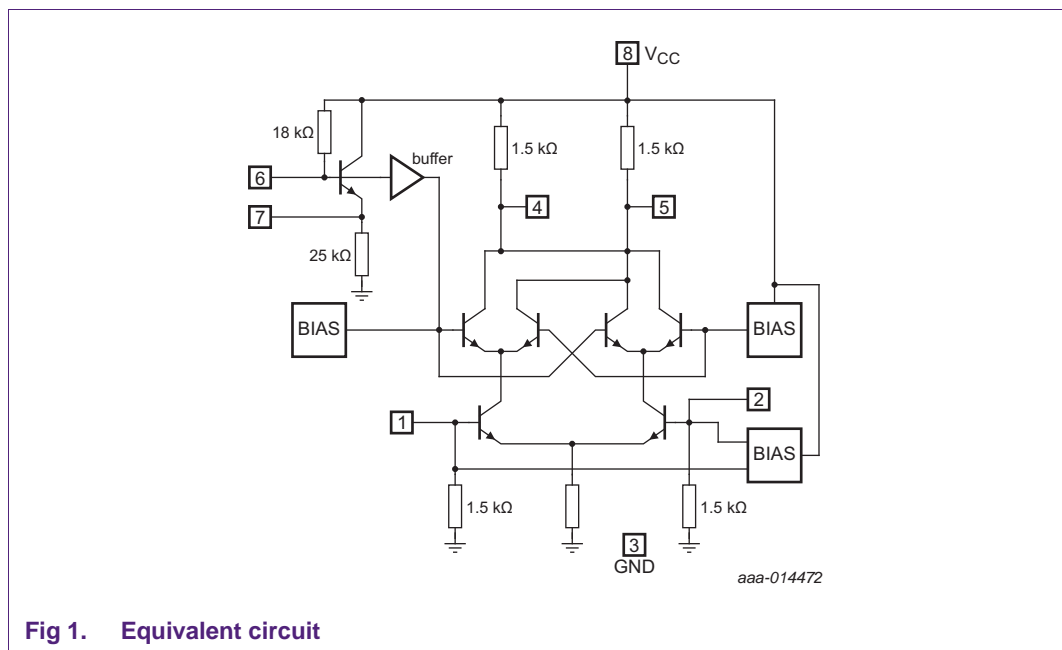


**Fig 1. Equivalent circuit**

While the oscillator is simple, oscillator design is not. This article will not address the rigors of oscillator design, but some practical guidelines will permit the designer to accomplish good performance with minimum difficulty.

Either crystal or LC tank circuitry can be employed effectively. [Figure 2](#) shows the four most commonly used configurations in their most basic form.

In each case, the Q of the tank will affect the upper frequency limits of oscillation: the higher the Q the higher the frequency. The SA602A is fabricated with a 6 GHz process, but the emitter resistor from Pin 7 to ground is nominally 20 kΩ. With 0.25 mA typical bias current, 200 MHz oscillation can be achieved with high Q and appropriate feedback.

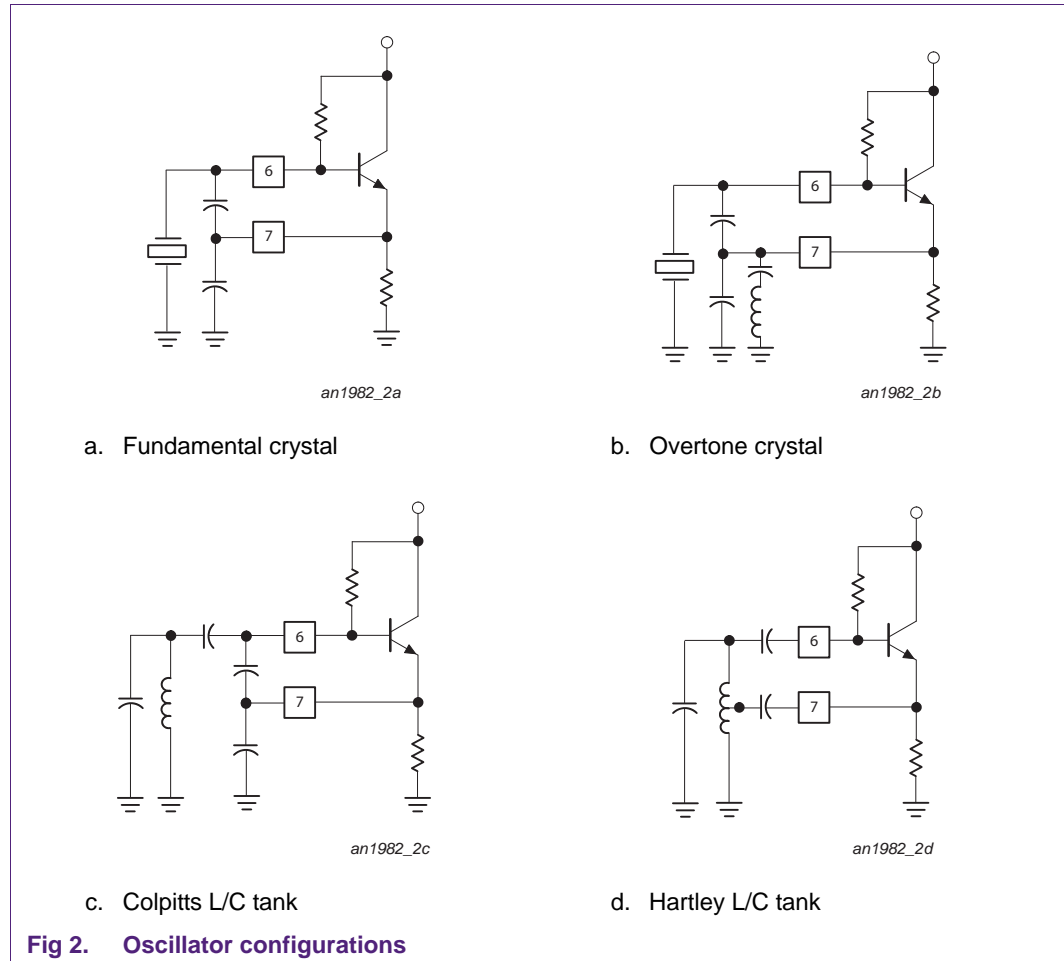The feedback, of course, depends on the Q of the tank. It is generally accepted that a minimum amount of feedback should be used, so even if the choice is entirely empirical, a good trade-off between starting characteristics, distortion, and frequency stability can be quickly determined.



## 2.1 Crystal circuit considerations

Crystal oscillators are relatively easy to implement since crystals exhibit higher Qs than LC tanks. [Figure 3](#) shows a complete implementation of the SA602A (extended temperature version) for cellular radio with a 45 MHz first IF and 455 kHz second IF.

The crystal is a third-overtone parallel mode with 5 pF of shunt capacitance and a trap to suppress the fundamental.

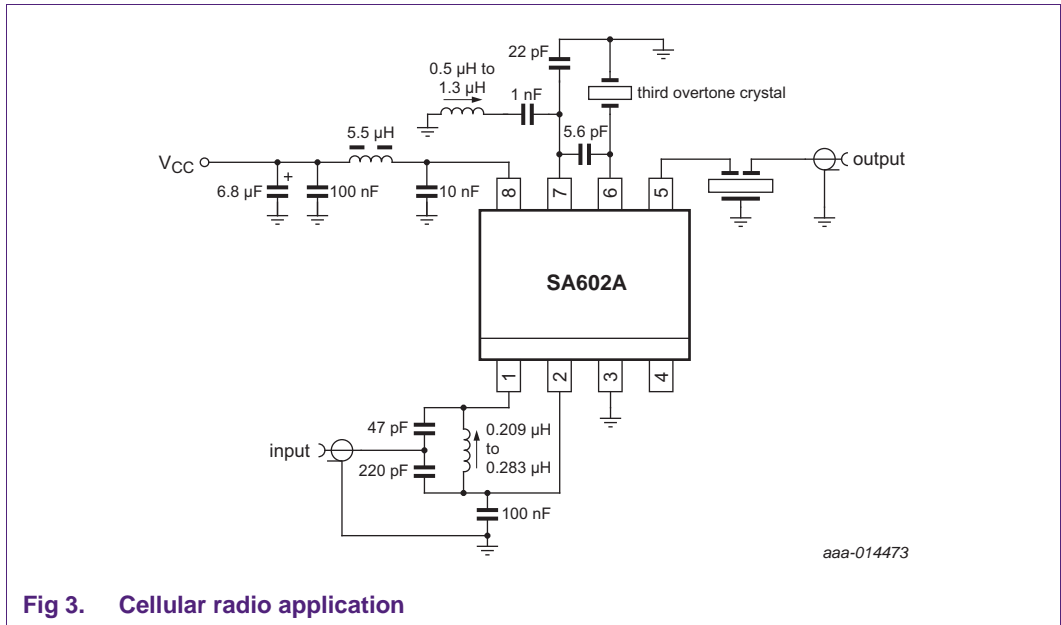


Fig 3. Cellular radio application

## 2.2 LC tank circuits

LC tanks present a little greater challenge for the designer. If the Q is too low, the oscillator will not start. A trick which will help if all else fails is to shunt Pin 7 to ground with a 22 kΩ resistor. In actual applications this has been effective to 200 MHz with high Q ceramic capacitors and a tank inductor of 0.08 μH and a Q of 90. Smaller resistor value will upset DC bias because of inadequate base bias at the input of the oscillator. An external bias resistor could be added from V<sub>CC</sub> to Pin 6, but this will introduce power supply noise to the frequency spectrum.


The Hartley configuration (Figure 2d) offers simplicity. With a variable capacitor tuning the tank, the Hartley will tune a very large range since all of the capacitance is variable. Note that the inductor must be coupled to Pin 7 with a low-impedance capacitor.

The Colpitts oscillator will exhibit a smaller tuning range since the fixed-feedback capacitors limit variable capacitance range; however, the Colpitts has good frequency stability with proper components.
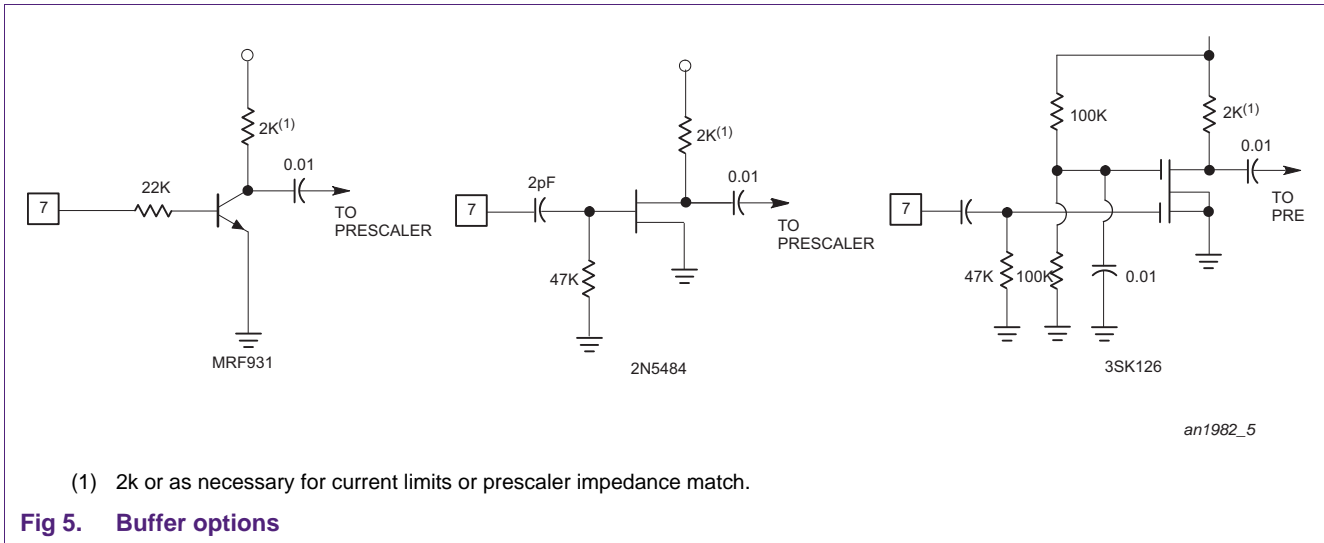
## 2.3 Synthesized frequency control

The SA602A can be very effective with a synthesizer if proper precautions are taken to minimize loading of the tank and the introduction of digital switching transients into the spectrum. Figure 4 shows a circuit suitable for aircraft navigation frequencies (108 MHz to 118 MHz) with 10.7 MHz IF.





The effectiveness of the MRF931 (or other VHF bipolar transistors) will depend on frequency and required input level to the prescaler. A bipolar transistor will generally provide the least isolation. At low frequencies the transistor can be used as an emitter-follower, but by VHF the base emitter junction will start to become a bidirectional capacitor and the buffer is lost.

The 2N5484 has an IDSS of 5 mA (max) and the 3SK126 has IDSS of 6 mA (max), making them suitable for low parts count, modest current buffers. The isolation is good.

### 2.4 Injected LO

If the application calls for a separate local oscillator, it is acceptable to capacitively-couple 200 mV to 300 mV at Pin 6.

## 3. Summary

The SA602A can be an effective low power mixer at frequencies to 500 MHz with oscillator operation to 200 MHz. All DC bias is provided internal to the device, so very compact designs are possible. The internal bias sets the oscillator DC current at a relatively low level, so the designer must choose frequency selective components which will not load the transistor. If the guidelines mentioned are followed, excellent results will be achieved.

## 4. Abbreviations

Table 1. Abbreviations

Acronym	Description
RF	Radio Frequency
LC	inductor-capacitor network
IF	Intermediate Frequency

Table 1. Abbreviations ...continued

Acronym	Description
MOSFET	Metal-Oxide Semiconductor Field-Effect Transistor
VHF	Very High Frequency
IDSS	drain-source saturation current ( $V_{GS} = 0\text{ V}$ )

## 5. References

- [1] **SA602A** — Product data sheet; NXP Semiconductors;  
[www.nxp.com/documents/data\\_sheet/SA602A.pdf](http://www.nxp.com/documents/data_sheet/SA602A.pdf)



## 6. Legal information

### 6.1 Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### 6.2 Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

**Right to make changes** — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected

to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Translations** — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

### 6.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

## 7. Contents

---

<b>1</b>	<b>Introduction</b> .....	<b>3</b>
<b>2</b>	<b>Description</b> .....	<b>3</b>
2.1	Crystal circuit considerations .....	4
2.2	LC tank circuits .....	5
2.3	Synthesized frequency control .....	5
2.4	Injected LO .....	7
<b>3</b>	<b>Summary</b> .....	<b>7</b>
<b>4</b>	<b>Abbreviations</b> .....	<b>7</b>
<b>5</b>	<b>References</b> .....	<b>8</b>
<b>6</b>	<b>Legal information</b> .....	<b>9</b>
6.1	Definitions .....	9
6.2	Disclaimers .....	9
6.3	Trademarks .....	9
<b>7</b>	<b>Contents</b> .....	<b>10</b>

---

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

---

© NXP Semiconductors N.V. 2014.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

Date of release: 29 August 2014

Document identifier: AN1982